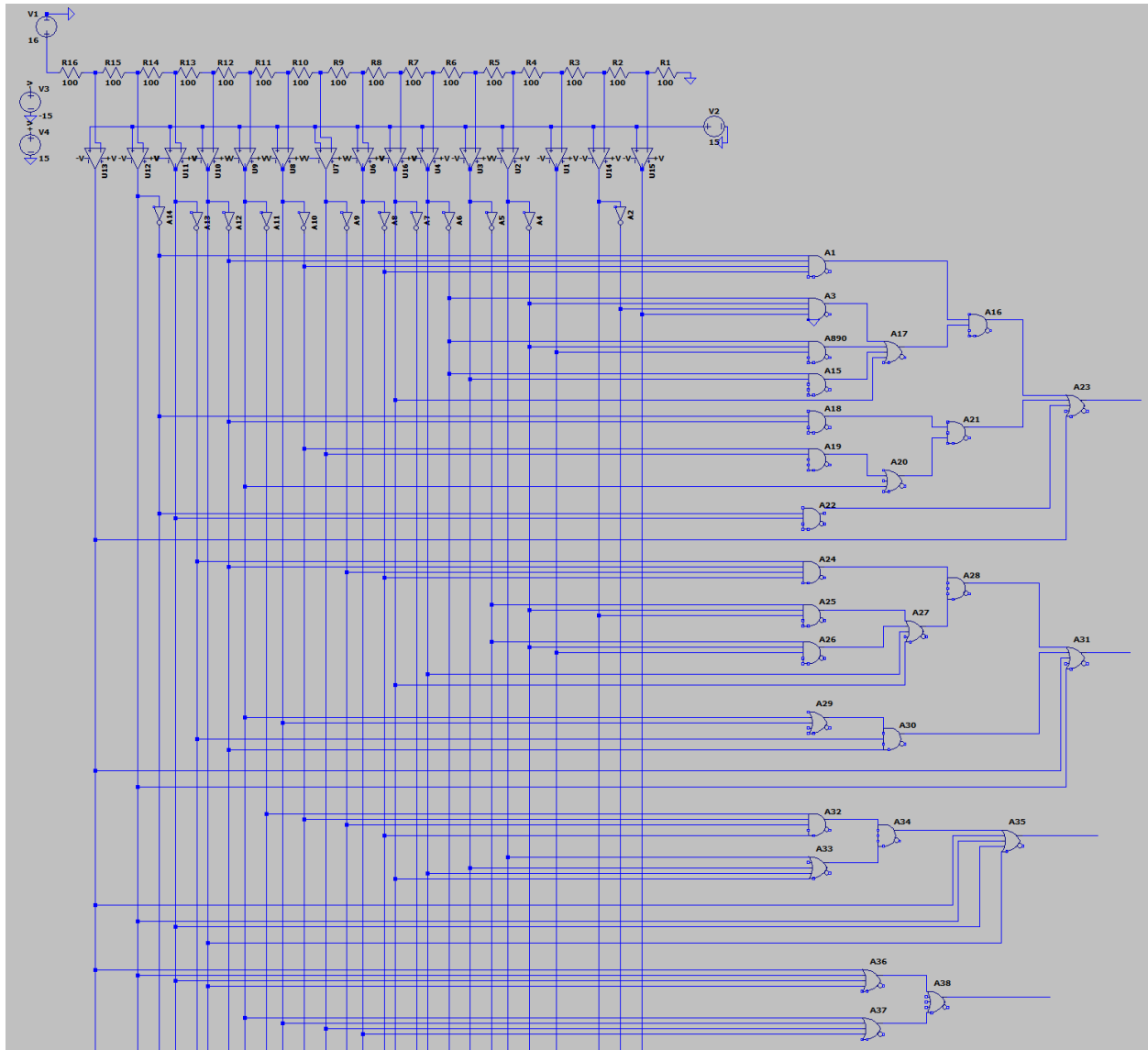


AIM: Simulating a flash ADC, and studying it's working and advantages.

In this report, we shall analyze how a flash ADC is made and will see the working of each component

Flash ADC simulation made in LTspice:



## Key Components of a 4-bit Flash ADC

### 1. Voltage Reference (Resistor Ladder Network)

- The resistor ladder consists  $2^4$  resistors (one for each reference voltage).
- It divides the input range into 16 levels.

## 2. Comparators

A 4-bit Flash ADC requires  $2^4 - 1$  **comparators**.

- Each comparator compares the input signal with a specific reference voltage from the resistor ladder.
- The output of each comparator is either high if the input voltage is above the reference or low if below.
- The comparator outputs form a thermometer code, where a sequenced of consecutive 1s indicate the input level.
- For a 4-bit Flash ADC, this code consists of 16 bits.

## 3. Encoder (Priority Encoder)

- A **4-bit priority encoder** converts the thermometer code into a 4-bit binary output.
- This encoder finds the highest active bit in the thermometer code and maps it to the corresponding binary output.
- It typically uses a multi-stage encoding process due to the large number of inputs.

The Priority Encoder is represented by the Boolean Expressions given below:

$$Y0 = \sum (\bar{D}_{14} \bar{D}_{12} \bar{D}_{10} \bar{D}_8 (\bar{D}_6 \bar{D}_4 \bar{D}_2 D_1 + \bar{D}_6 \bar{D}_4 D_3 + \bar{D}_6 D_5 + D_7) + \bar{D}_{14} \bar{D}_{12} (\bar{D}_{10} D_9 + D_{11}) + \bar{D}_{14} D_{13} + D_{15})$$

$$Y1 = \sum (\bar{D}_{13} \bar{D}_{12} \bar{D}_9 \bar{D}_8 (\bar{D}_5 \bar{D}_4 D_2 + \bar{D}_5 \bar{D}_4 D_3 + D_6 + D_7) + \bar{D}_{13} \bar{D}_{12} (D_{10} + D_{11}) + D_{14} + D_{15})$$

$$Y2 = \sum (\bar{D}_{11} \bar{D}_{10} \bar{D}_9 \bar{D}_8 (D_4 + D_5 + D_6 + D_7) + D_{12} + D_{13} + D_{14} + D_{15})$$

$$Y3 = \sum (D_8 + D_9 + D_{10} + D_{11} + D_{12} + D_{13} + D_{14} + D_{15})$$

Y0, Y1, Y2 and Y3 are the 4 output bits with Y3 being the most significant bit and Y0 being the least significant bit. D1 to D15 are the thermometer code.

## How a Flash ADC Works

1. Analog Input
  - The analog signal  $V_{in}$  is fed into all the comparators simultaneously.
2. Comparison Against Reference Levels
  - Each comparator checks whether  $V_{in}$  is greater than its assigned reference voltage from the resistor ladder.
  - The comparators whose reference voltages are  $V_{in}$  output high, while those above  $V_{in}$  output low.
3. Thermometer Code Generation
  - The comparators produce a thermometer code.
  - For example,  $V_{in}$  corresponds to the 7th level in an 16-level ADC:
    - Output = 000000001111111.
4. Encoding
  - The thermometer code is passed through a priority encoder to produce the digital output.
  - For the above example:
    - Thermometer Code: 000000001111111
    - Encoded Binary Output: 0111 (binary for 7).

### Working of the simulation:

Now let's test the simulation by giving a specific DC voltage input:

Let  $V_{in} = 7\text{ V}$



LTspice -  
4bit\_flash\_adc 2024-1

The video above shows the output when we give the input voltage as 7V.

Let  $V_{in} = 10\text{ V}$



LTspice -  
4bit\_flash\_adc 2024-1

The video above shows the output when we give the input voltage as 10V.

### **Advantages of Flash ADC:**

1. Flash ADCs are the fastest type of ADC, making them ideal for applications requiring very high sampling rates.
2. Simple Operational Concept: The design relies on basic components: resistors, comparators, and an encoder
3. Continuous Conversion: Flash ADCs perform a continuous, real-time conversion of the analog input to digital output, which is crucial in systems requiring minimal delay.
4. At resolutions below 8 bits, the simplicity of Flash ADCs can lead to lower power consumption compared to other ADC types.

### **Disadvantages of Flash ADC:**

1. Exponential Component Growth: For an  $N$ -bit resolution, a Flash ADC requires  $2^N - 1$  comparators and  $2^N$  resistors in the resistor ladder.  
This exponential growth increases the circuit complexity, size, and cost.
2. High Power Consumption: With a large number of comparators operating simultaneously, Flash ADCs consume significantly more power than other ADC types.
3. Poor Resolution: While fast, Flash ADCs are generally not used for resolutions greater than 8–10 bits due to their impracticality.